Voltage Sensor Analysis

Prepared by Siddhart Patel

November 19, 2024

Contents


1	Introduction	2
2	Circuit Diagram	2
3	Voltage Divider Formula	2
4	Resistor Selection	2
5	Experimental Observations	2
6	Verification of Factor	3
7	Conclusion	3

1 Introduction

This document provides an analysis of a simple voltage sensor circuit based on a voltage divider configuration. The sensor reduces the input voltage (V_{in}) to a lower voltage (V_{out}) that can be safely read by a microcontroller such as an Arduino.

2 Circuit Diagram

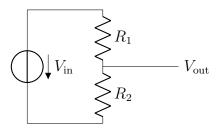The voltage divider circuit used in the sensor is shown below:



3 Voltage Divider Formula

The output voltage of the circuit is determined by the voltage divider formula:

$$V_{\rm out} = V_{\rm in} \times \frac{R_2}{R_1 + R_2}$$

4 Resistor Selection

From the calculation:

$$Factor = \frac{R_2}{R_1 + R_2}$$

Given:

$$Factor = 0.2$$

and resistors:

$$R_1 = 30k\Omega, \quad R_2 = 7.5k\Omega$$

Substitute into the equation:

$$0.2 = \frac{7.5 \text{k}\Omega}{30 \text{k}\Omega + 7.5 \text{k}\Omega}$$

5 Experimental Observations

• Input voltage $(V_{\rm in})$ from the adapter: 12.11 V

• Output voltage (V_{out}) read on the Arduino: 5.06 V

• Voltage reference on Arduino ($V_{\rm CC}$): 5.06 V

6 Verification of Factor

The factor for the voltage divider can also be determined as:

$$Factor = \frac{V_{in}}{V_{out}}$$

Substituting the values:

$$Factor = \frac{12.11}{5.06} \approx 2.43$$

Key Observation

The calculated factor matches the expected division ratio, validating the resistor selection and circuit performance.

7 Conclusion

The voltage sensor successfully scales down the input voltage to a level that is readable by the Arduino. The calculated and measured values demonstrate consistency, and the voltage divider circuit provides a simple yet effective solution for voltage measurement in microcontroller-based applications.